

Department of Computer Science & Engineering (CSE)

---

# Course Title: Digital Logic Design

Shahriar Rahman Khan

Lecturer

Dept. of CSE, MIST

Course Code: CSE 103

Credit Hr: 3.00

Contact Hr: 3.00



# Overview

---

- What is MSI and PLD?
- Binary parallel Adder
- Binary Adder-Subtractors
- Carry Propagation
- BCD Adder
- Magnitude Comparator
- Decoders and De-multiplexers
- Encoders and Multiplexers
- Priority Encoders



# Magnitude Comparator

---

- The comparison of two numbers is an operation that determines if one number is greater than, less than or equal to the other number.
- A magnitude comparator is a combinational circuit that compares two numbers A and B.
- The outcome of the comparison is specified by 3 binary variables that indicate whether  $A > B$ ,  $A = B$  or  $A < B$



# Magnitude Comparator: $A=B$

---

Consider two numbers, A and B

- $A=A_3 A_2 A_1 A_0$
- $B=B_3 B_2 B_1 B_0$
- Now, two numbers are equal if  $A_3=B_3$  and  $A_2=B_2$  and  $A_1=B_1$  and  $A_0=B_0$
- As the numbers are binary, the digits are either 0 or 1.
- Let,  $A = 1011$ ,  $B = 1011$
- $A_3=B_3=1$  or  $A_3'=B_3'=1$
- $x_i = A_i B_i + A_i' B_i' = A_i \text{ xnor } B_i$  ;where,  $i=0,1,2,3$
- Let  $i=0$
- $x_0$  will be equal to 1 if either  $(A_0 = B_0 = 1)$  or  $(A_0 = B_0 = 0)$
- So,  $x_0 = A_0 B_0 + A_0' B_0'$
- Same for  $x_3, x_2$ , and  $x_1$
- Finally,  $(A=B) = x_3 x_2 x_1 x_0$



# Magnitude Comparator: $A > B$

Consider two numbers, A and B

- $A = A_3 A_2 A_1 A_0$
- $B = B_3 B_2 B_1 B_0$
- Now,  $A > B$  if
  - $A_3 > B_3$  or
  - $A_3 = B_3$  and  $A_2 > B_2$  or
  - $A_3 = B_3$  and  $A_2 = B_2$  and  $A_1 > B_1$  or
  - $A_3 = B_3$  and  $A_2 = B_2$  and  $A_1 = B_1$  and  $A_0 > B_0$

- Let,  $A = 1110$ ,  $B = 0010$

- Now, as we know
- $x_i = A_i B_i + A_i' B_i' = A_i \text{ xnor } B_i$  ; where,  $i=0,1,2,3$
- $(A_0 = B_0) = x_0 = A_0 B_0 + A_0' B_0'$
- $(A_1 = B_1) = x_1 = A_1 B_1 + A_1' B_1'$
- $(A_2 = B_2) = x_2 = A_2 B_2 + A_2' B_2'$
- $(A_3 = B_3) = x_3 = A_3 B_3 + A_3' B_3'$
- Finally,  $(A > B) = A_3 B_3' + x_3.A_2 B_2' + x_3.x_2.A_1 B_1' + x_3.x_2.x_1.A_0 B_0'$



# Magnitude Comparator: $A < B$

Consider two numbers, A and B

- $A = A_3 A_2 A_1 A_0$
- $B = B_3 B_2 B_1 B_0$
- Now,  $A < B$  if
  - $A_3 < B_3$  or
  - $A_3 = B_3$  and  $A_2 < B_2$  or
  - $A_3 = B_3$  and  $A_2 = B_2$  and  $A_1 < B_1$  or
  - $A_3 = B_3$  and  $A_2 = B_2$  and  $A_1 = B_1$  and  $A_0 < B_0$
- Let,  $A = 1001$ ,  $B = 1011$
- Now, as we know,
- $x_i = A_i B_i + A_i' B_i' = A_i \text{ xnor } B_i$  ;where,  $i=0,1,2,3$
- $(A_0 = B_0) = x_0 = A_0 B_0 + A_0' B_0'$
- $(A_1 = B_1) = x_1 = A_1 B_1 + A_1' B_1'$
- $(A_2 = B_2) = x_2 = A_2 B_2 + A_2' B_2'$
- $(A_3 = B_3) = x_3 = A_3 B_3 + A_3' B_3'$
- Finally,  $(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$

# Magnitude Comparator

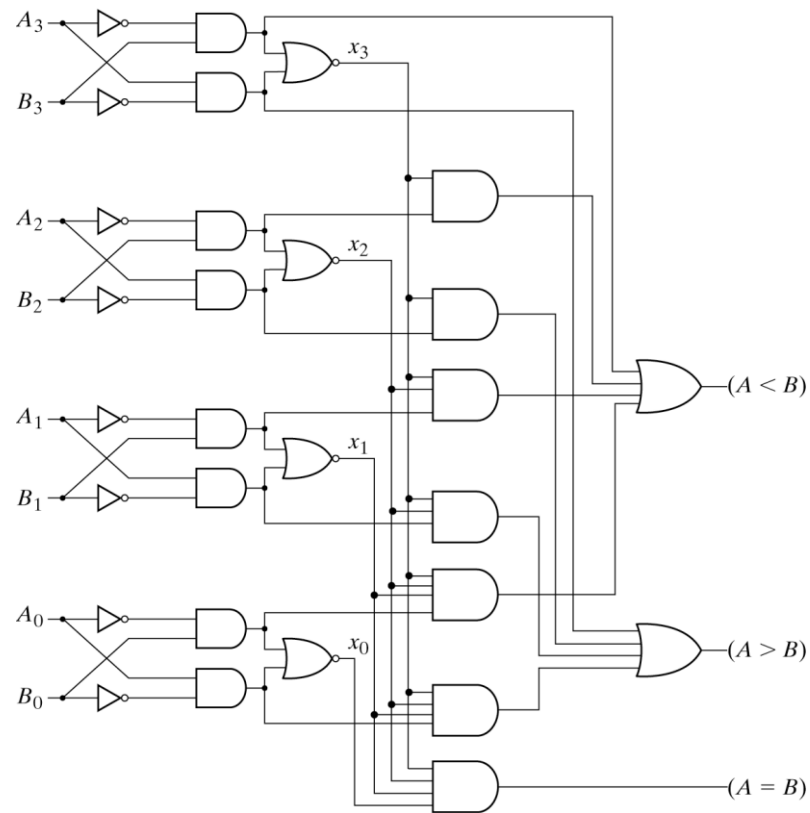



Fig. 4-17 4-Bit Magnitude Comparator



GOOD NEWS!  
THE CLASS IS  
OVER...  
THANK YOU!