

Department of Computer Science & Engineering (CSE)

---

# Course Title: Digital Logic Design

Shahriar Rahman Khan

Lecturer

Dept. of CSE, MIST

Course Code: CSE 103

Credit Hr: 3.00

Contact Hr: 3.00




# Overview

---

- What is MSI and PLD?
- Binary parallel Adder
- Binary Adder-Subtractors
- Carry Propagation
- BCD Adder
- Magnitude Comparator
- Decoders and De-multiplexers
- Encoders and Multiplexers
- Priority Encoders

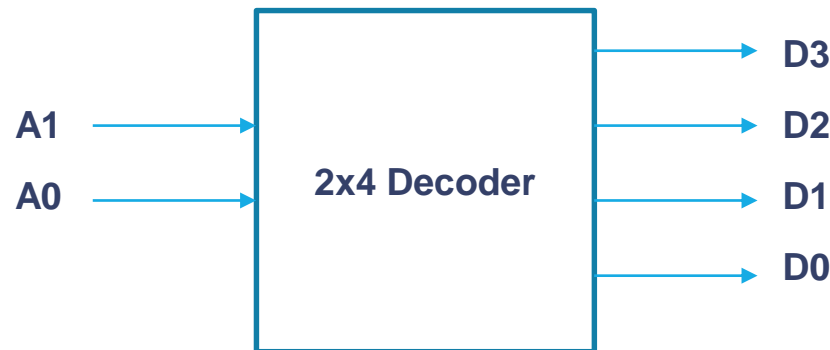
# Decoder

- We know, discrete quantities of information are represented in digital systems with binary codes.
- A binary code of  $n$  bits is capable of representing up to  $2^n$  distinct elements of the coded information. Let you can represent 8 distinct elements of coded information using 3 bits as  $2^3 = 8$ .
- A decoder is a combinational circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  output lines.


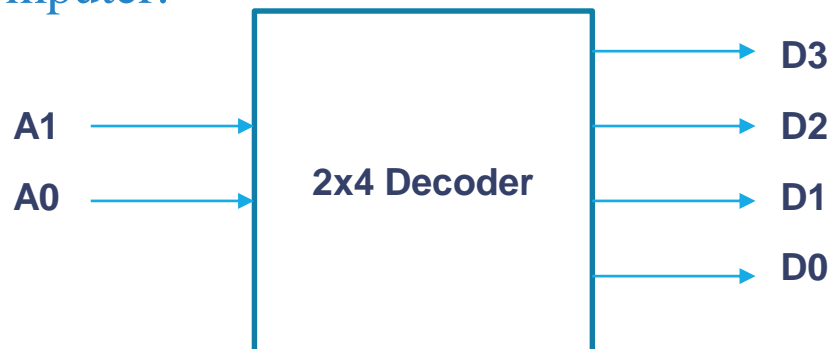
# Decoder

- A computer is connected with 4 output devices, let's say printers. Now a computer operator will select a printer among the 4 printers. To do that, he has to give input to his computer.




- How many bits required to select any 1 printer among the 4 printers?

A1	A0	D3	D2	D1	D0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0
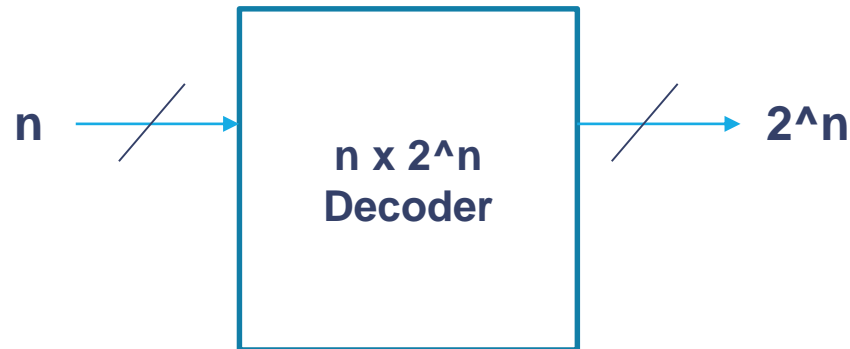
# Decoder

- A combinational circuit that produces  $2^n$  output lines, in response of  $n$  input lines



- Configuration of a Decoder: No of input lines x No of output lines
- So, generalized configuration of a Decoder: If there are  $n$  input lines then, Decoder would be  $n \times 2^n$  Decoder.
- If, the  $n$  bit decoded information has unused don't care combinations, then the decoder output will have less than  $2^n$  output lines. Let,  $m$  = no of output lines, where  $m \leq 2^n$ .
- So, a decoder is also called  $n$ -to- $m$ -line decoder. Like, 3-to-8-line decoder.



# Use of Decoder

---

- The purpose of a decoder is to generate  $2^n$  (or fewer) minterms of  $n$  input variables.
- It is used to convert binary data to other codes. Example: binary to octal code conversion, BCD to decimal code conversion, binary to hexadecimal code conversion.
- Decoders are used to input data to a specified output line as is done in addressing core memory where input data is to be stored in a specified memory location.
- It may also be used for data distribution i.e. De-multiplexing.



# 3-to-8-line Decoder

---

- In the 3-to-8-line decoder circuit, the 3 inputs are decoded into 8 outputs, where each output representing 1 of the minterms of the 3 input variables.
- A particular application of this circuit is binary-to-octal conversion.
- The input variables may represent a binary number, where the outputs will then represent the 8 digits in the octal number system.

# 3-to-8-line Decoder


**Truth Table of a 3-to-8-Line Decoder**

Inputs			Outputs							
$x$	$y$	$z$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

- If you observe the truth table, you can see the output variables are mutually exclusive because only one output can be equal to 1 at any one time.
- We can represent any function using a decoder.



# 3-to-8-line Decoder

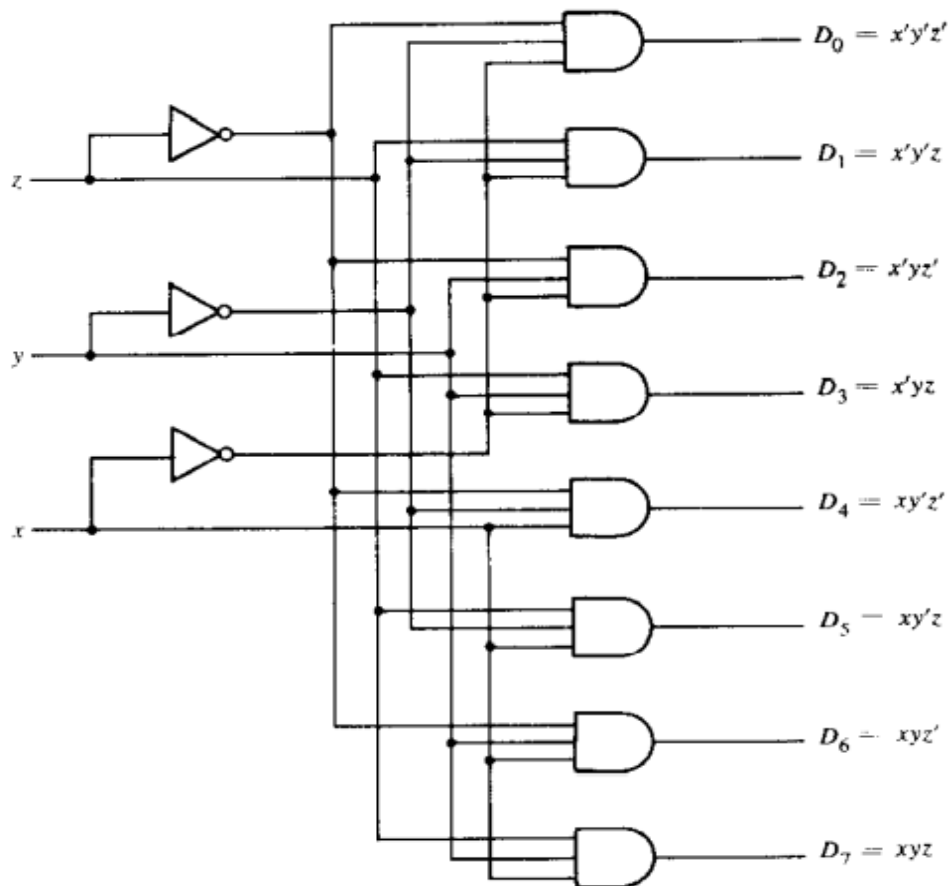



# BCD-to-Decimal Decoder

---

- In the BCD-to-Decimal code conversion, 4-to-10-line decoder circuit is used, the 4 inputs are decoded into 10 (0-9) outputs, where each output representing 1 of the minterms of the 4 input variables.
- The input variables may represent a binary number, where the outputs will then represent the 10 digits in the decimal number system.

# BCD-to-Decimal Decoder

BCD				Decimal									
$A$	$B$	$C$	$D$	$D_9$	$D_8$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	0	0	1	0	0	0
0	1	0	0	0	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	1	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	1	0	0	0	0	0	0	0	0	0


# BCD-to-Decimal Decoder

<b>CD AB</b>	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>00</b>	D0	D1	D3	D2
<b>01</b>	D4	D5	D7	D6
<b>11</b>	X	X	X	X
<b>10</b>	D8	D9	X	X

Instead of drawing 10 k-maps, we are drawing only one and write each of the output variables.

- $D0 = A'B'C'D'$
- $D1 = A'B'C'D$
- $D2 = B'CD'$
- $D3 = B'CD$
- $D4 = BC'D'$
- $D5 = BC'D$
- $D6 = BCD'$
- $D7 = BCD$
- $D8 = AD'$
- $D9 = AD$

# BCD-to-Decimal Decoder

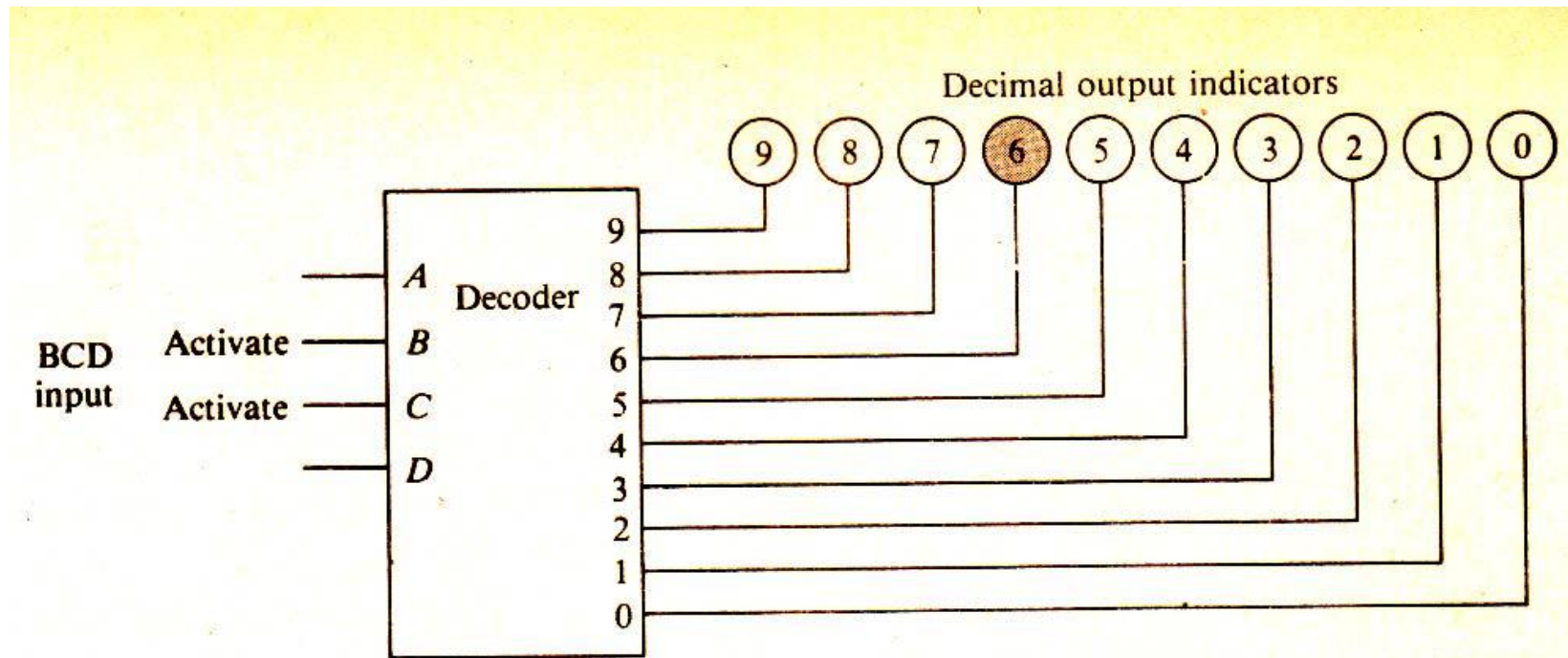

**Fig. 6-6** Logic symbol for a BCD-to-decimal decoder



# Combinational Logic Implementation using Decoder

---

- As we know, a decoder provides the  $2^n$  minterms of  $n$  input variables.
- Also, we know, any Boolean function can be expressed in sum of minterms canonical form.
- So one can use a decoder to generate the minterms and an external OR gate to form the sum.
- The Boolean functions expressed in sum of minterms, can be obtained by forming the truth table or by expanding the functions to their sum of minterms.
- Let,  $F(A,B,C) = AB' + BC + A'C'$

# Full-Adder using Decoder

You remember this combinational circuit named Full-Adder from chap 4. As this is a combinational circuit that adds three 1 bit binary digits, so there will be 3 input variables and 2 output variables.

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Full-Adder using Decoder

0	1	0	1
1	0	1	0

0	0	1	0
0	1	1	1

$$S(x, y, z) = \Sigma(1, 2, 4, 7)$$

$$C(x, y, z) = \Sigma(3, 5, 6, 7)$$



# Full-Adder using Decoder

$$S(x, y, z) = \Sigma(1, 2, 4, 7)$$

$$C(x, y, z) = \Sigma(3, 5, 6, 7)$$

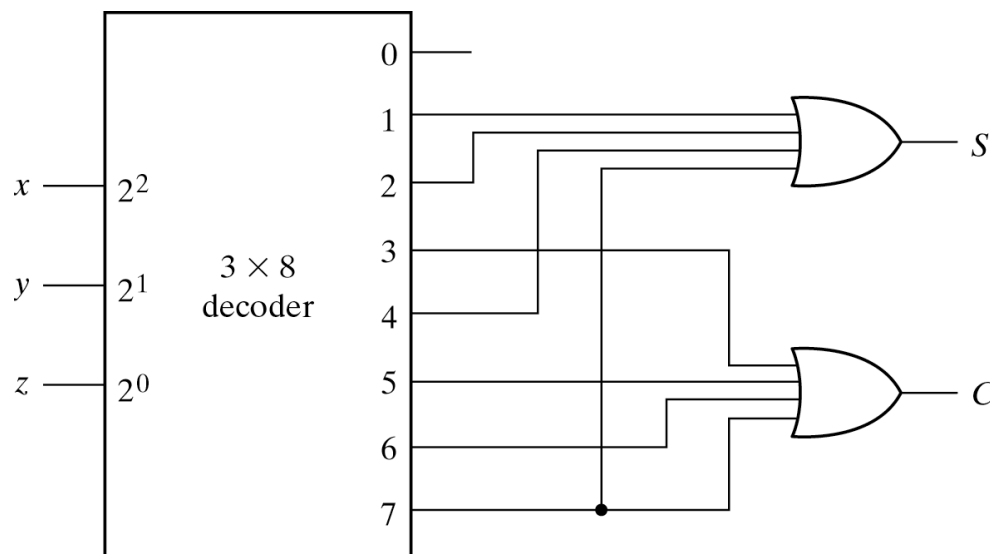


Fig. 4-21 Implementation of a Full Adder with a Decoder

# Combinational Logic

## Implementation using Decoder

- Now, if there is a function with a long list of minterms, then it will be required an OR gate with a large number of inputs.
- A function  $F$  having a list of  $k$  minterms can be expressed in its complemented form  $F'$ .


- Let  $F = \Sigma(0,1,5,6,7)$
- $F = m_0 + m_1 + m_5 + m_6 + m_7$
- $F' = m_2 + m_3 + m_4$
- $F = (F')'$
- $F = (m_2 + m_3 + m_4)'$
- $\text{NOR}(m_2, m_3, m_4)$

- Hence, the decoder method can be used  
To implement any combinational circuit.

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

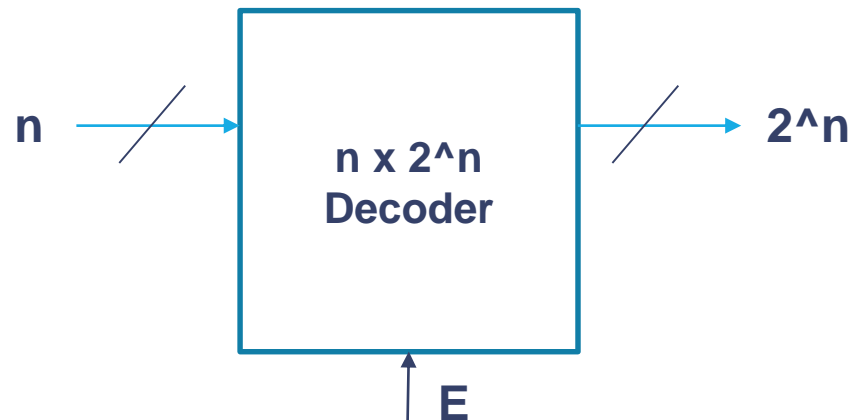
# Decoder with Enable Pin

- Now, we introduce Enable pin E in a decoder. On the value of E, the decoder activates.
- There can be two types of activation: 1-activation and 0-activation.
- In 1-activation, the decoder activates, when  $E=1$  and decoder will be disabled, when  $E=0$ .
- In 0-activation, the decoder activates, when  $E=0$  and decoder will be disabled, when  $E=1$ .


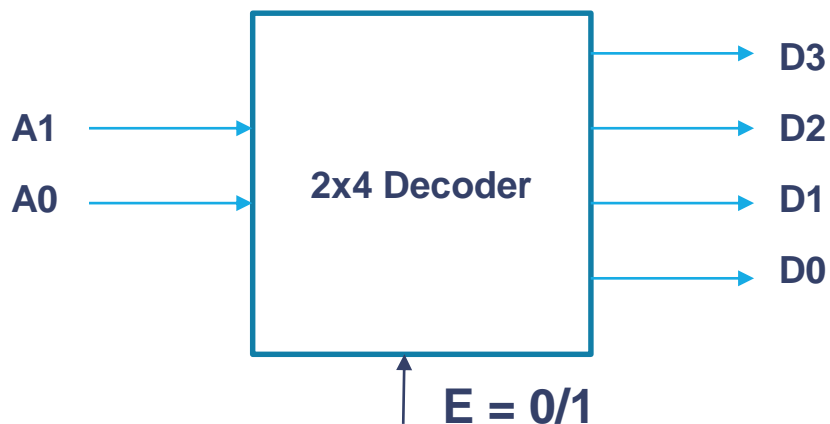
# Decoder with 1-activation


- In 1-activation, the decoder activates, when  $E=1$  and decoder will be disabled, when  $E=0$ .



E	A1	A0	D3	D2	D1	D0
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

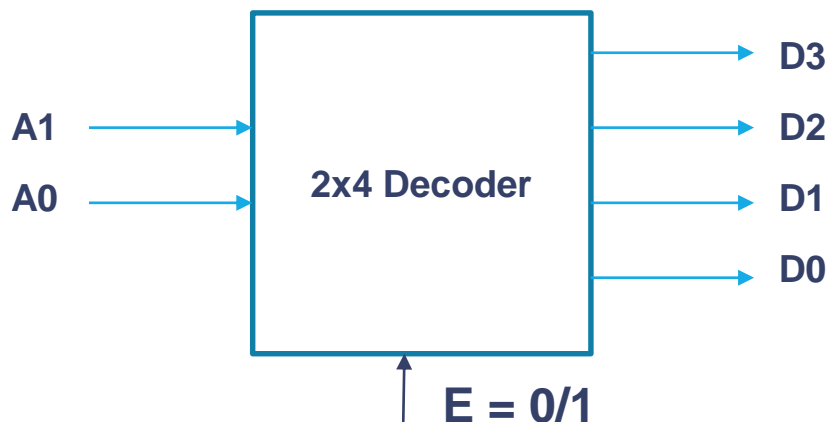
# Decoder with 0-activation

- In 0-activation, the decoder activates, when  $E=0$  and decoder will be disabled, when  $E=1$ . 0-activation decoder is used much more than 1-activation. Because, you can implement the outputs using NAND gates and NAND gate is universal.



E	A1	A0	D3	D2	D1	D0
1	X	X	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

# Decoder with 0-activation

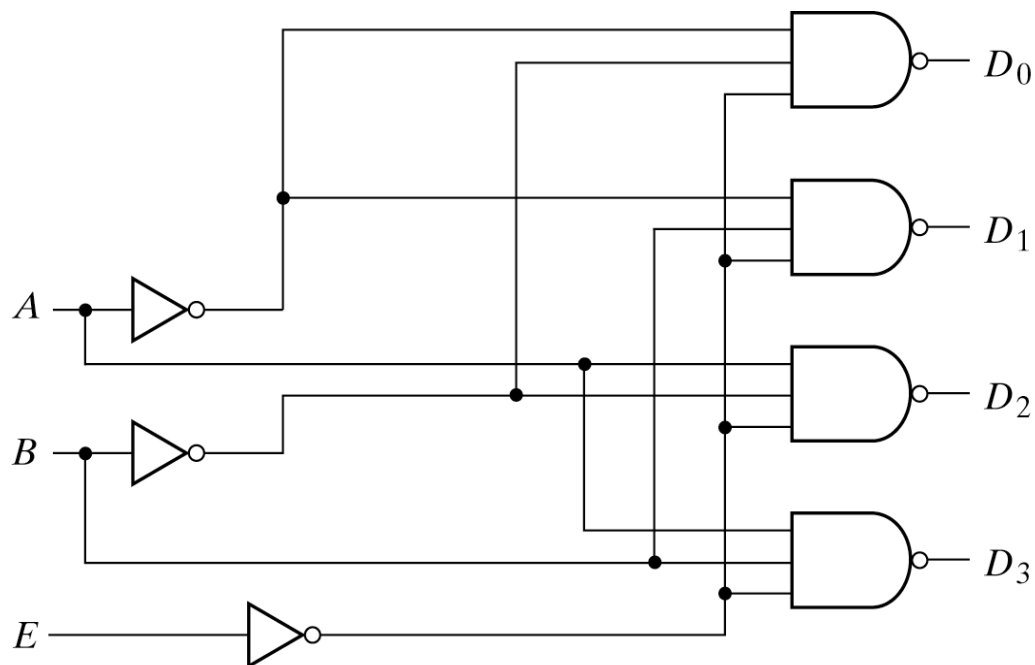

(a) Logic diagram

$E$	$A$	$B$	$D_0$	$D_1$	$D_2$	$D_3$
1	$X$	$X$	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

# Decoder with 0-activation

A0A1		00	01	11	10
E	0	0	1	1	1
	1	1	1	1	1

- $D0' = E'A0'A1'$
- $D0 = (E'A0'A1')'$
- Same for D1, D2, and D3
- This can be implemented using NAND gate, that's why in the logic diagram, NAND gate is used. Also, as NAND gate is universal, that's why 0-activation is much more used than 1-activation


# 3x8 Decoder using 2x4 Decoder

- Now to implement a 3x8 decoder using 2x4 decoder, we can use the enable pin E.

			Decoder-2				Decoder-1			
A2 (E)	A1	A0	D7	D6	D5	D4	D3	D2	D1	D0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0



# 3x8 Decoder using 2x4 Decoder

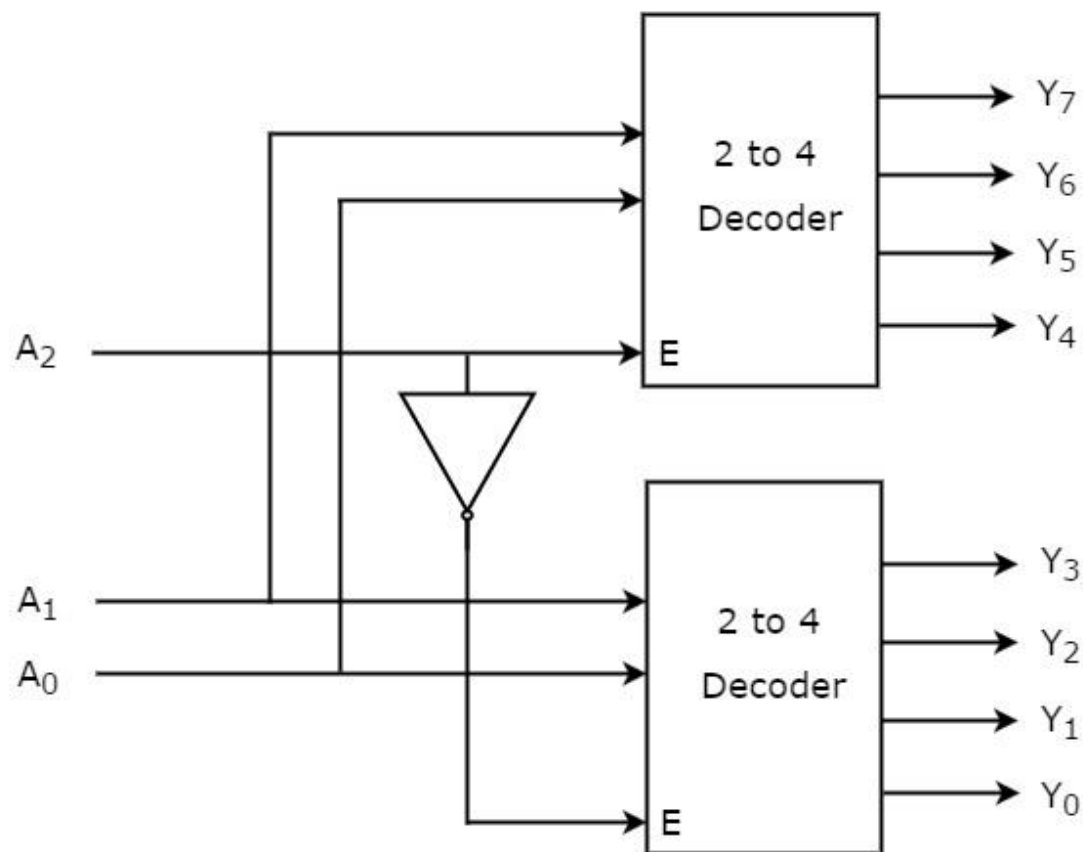




# De-multiplexer

---

- Now, a decoder with an enable input can function as a de-multiplexer.
- A de-multiplexer is a circuit that receives information on a single line and transmits this information on one of  $2^n$  possible output lines.
- The selection of a specific output line is controlled by the  $n$  selection lines.
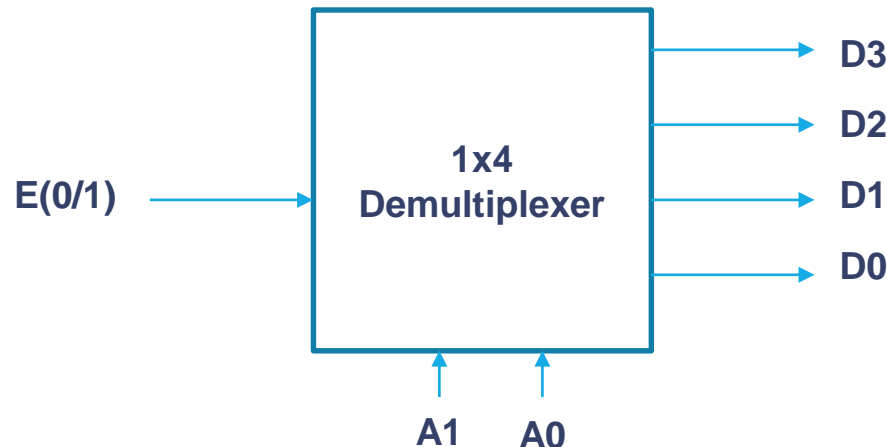
# De-multiplexer

- Remember the example, A computer is connected with 4 output devices, let's say printers. Now a computer operator will select a printer among the 4 printers. To do that, he has to give input to his computer. So far we have done this using decoder.
- So, we have selected the printer, now we need to print a document. How to pass the document or data to the printer? We do this using data line E.
- So we can say that, a decoder with an enable input can function as a de-multiplexer. This is also called decoder/de-multiplexer.






# Decoder as De-multiplexer


---

- So, a decoder with an enable input can function as a de-multiplexer.
- A de-multiplexer is a circuit that receives information on a single line and transmits this information on one of  $2^n$  possible output lines.
- The selection of a specific output line is controlled by the  $n$  selection lines.
- Everything is like decoder. When you select  $A_1A_0=00$ , then  $D_0$  printer becomes activated and the data  $E$  will pass to the output and  $D_0$  printer will print it.
- When you select  $A_1A_0=10$ , then  $D_2$  printer becomes activated and the data  $E$  will pass to the output and  $D_2$  printer will print it.

# Decoder as De-multiplexer

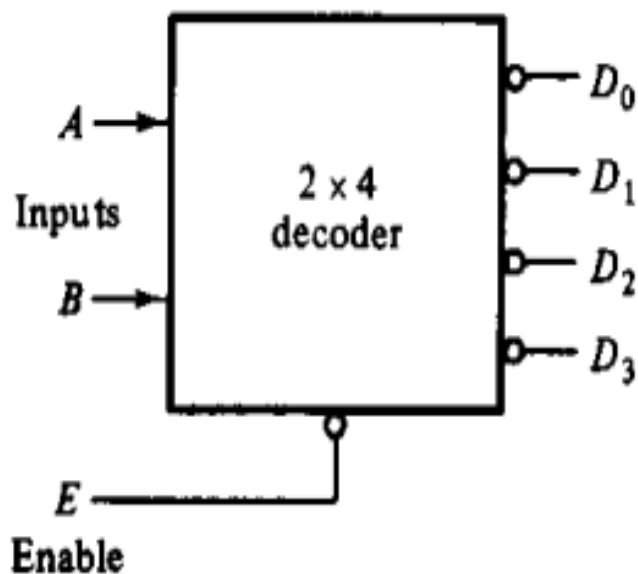

(a) Decoder with enable

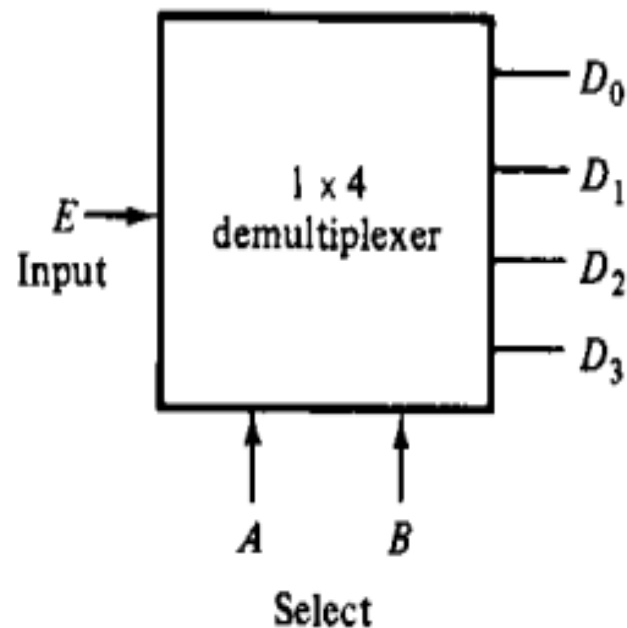

(b) Demultiplexer

# De-multiplexer

E	A1	A0	D3	D2	D1	D0
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

A1	A0	D3	D2	D1	D0
0	0	0	0	0	E
0	1	0	0	E	0
1	0	0	E	0	0
1	1	E	0	0	0

# De-multiplexer

Now, in the truth table have we ever seen that output is a variable?

No!

So, what we will do is, we will write the functions like this:

A1	A0	D3	D2	D1	D0
0	0	0	0	0	E
0	1	0	0	E	0
1	0	0	E	0	0
1	1	E	0	0	0

- $D0 = A1'A0'E$
- Here, D0 will be 1, when E=1. We are considering only that case, because always remember, a Boolean function will give output 1.
- $D1 = A1'A0E$
- $D2 = A1A0'E$
- $D3 = A1A0E$



# De-multiplexer


---

- So, if no of outputs,  $n=2^m$
  - Then,  $m$ =no of selection lines.
  - Here,  $n=4$ , so  $m=2$
- 
- Types: 1:2 DEMUX, 1:4 DEMUX, 1:8 MUX, 1:16 DEMUX, 1:32 DEMUX



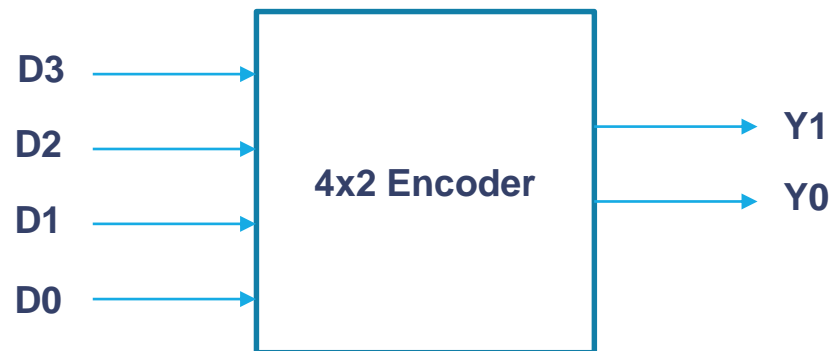
# Encoder

- An encoder is a digital circuit that performs the inverse operation of a decoder.
- It has  $2^n$  (or fewer) input lines and  $n$  output lines.
- It generates binary code corresponding to the input lines.
- Example, Octal-to-Binary code converter.




# Octal-to-Binary Encoder

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

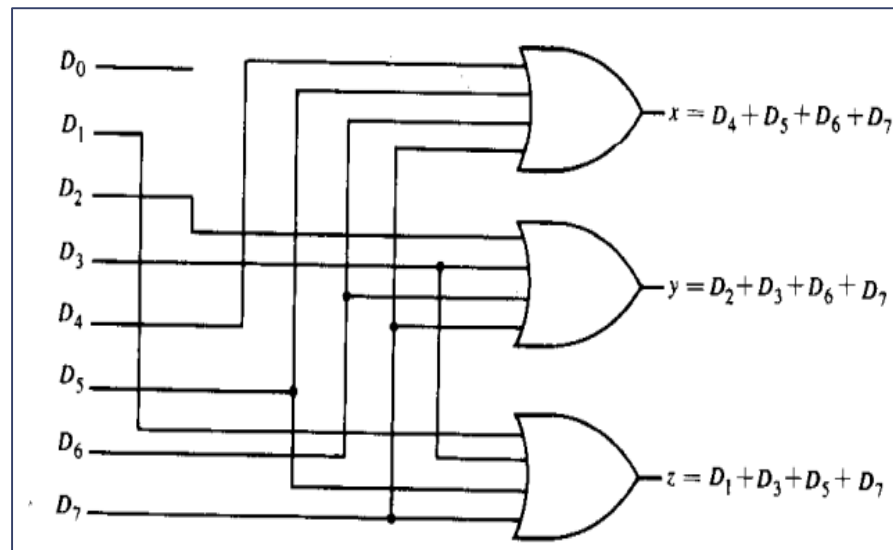


# Octal-to-Binary Encoder

---

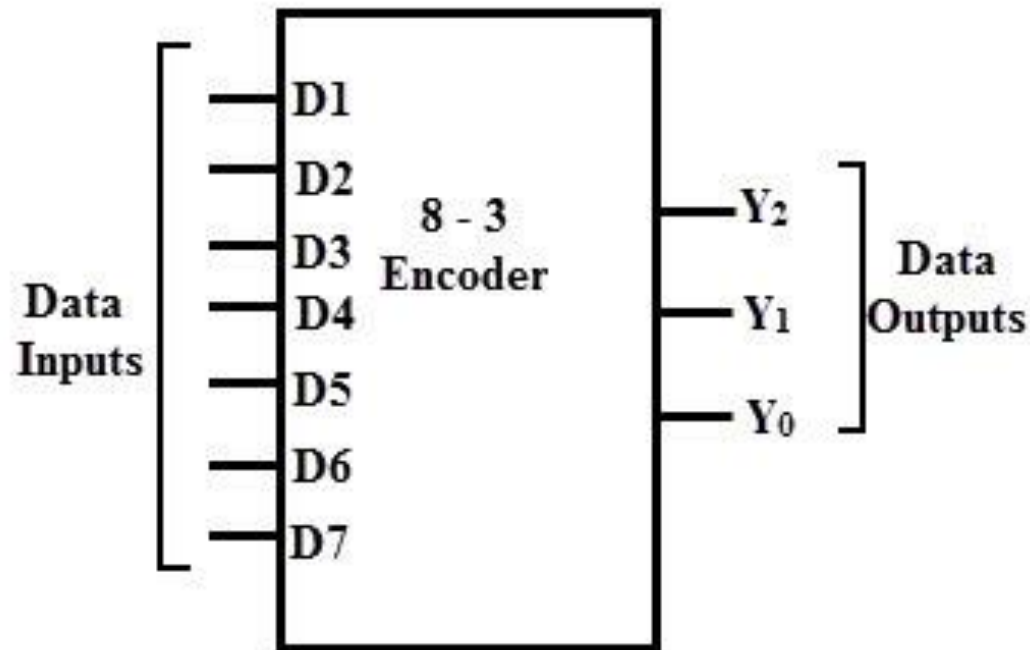

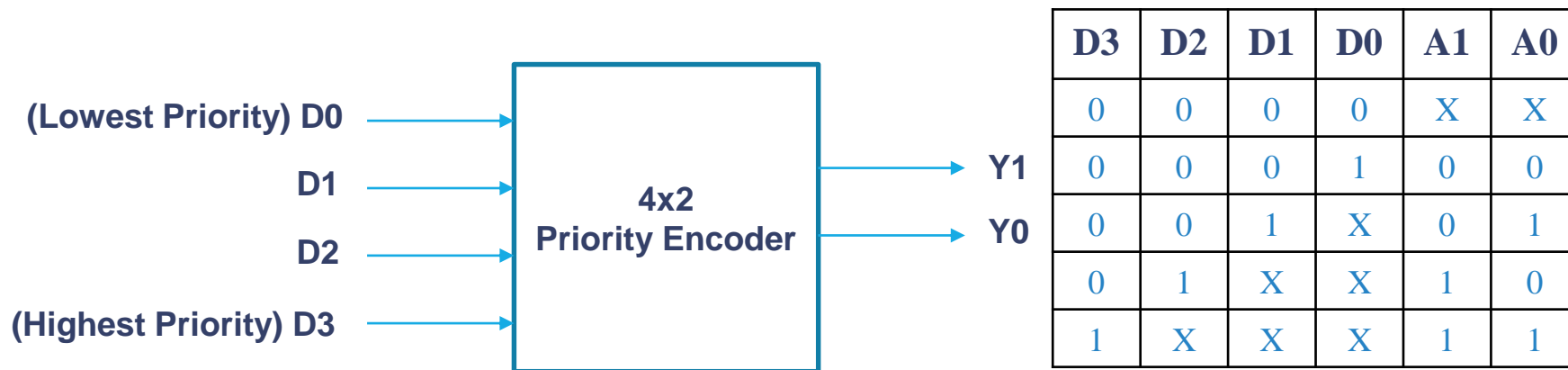
# Priority Encoder


- A priority encoder is a digital circuit that includes the priority function.
- The operation of the priority encoder is such that, if two or more inputs are equal to 1 at the same time, then the input having the highest priority will take precedence.



# Priority Encoder

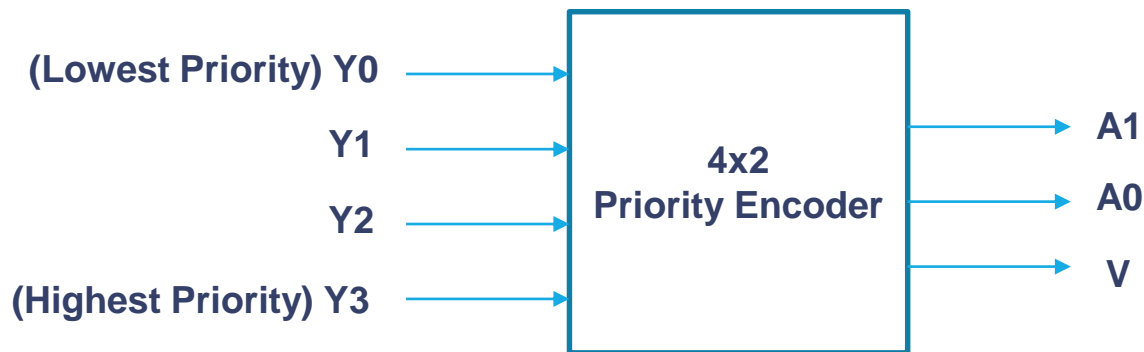


$Y_3$	$Y_2$	$Y_1$	$Y_0$	$A_1$	$A_0$	$V$
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

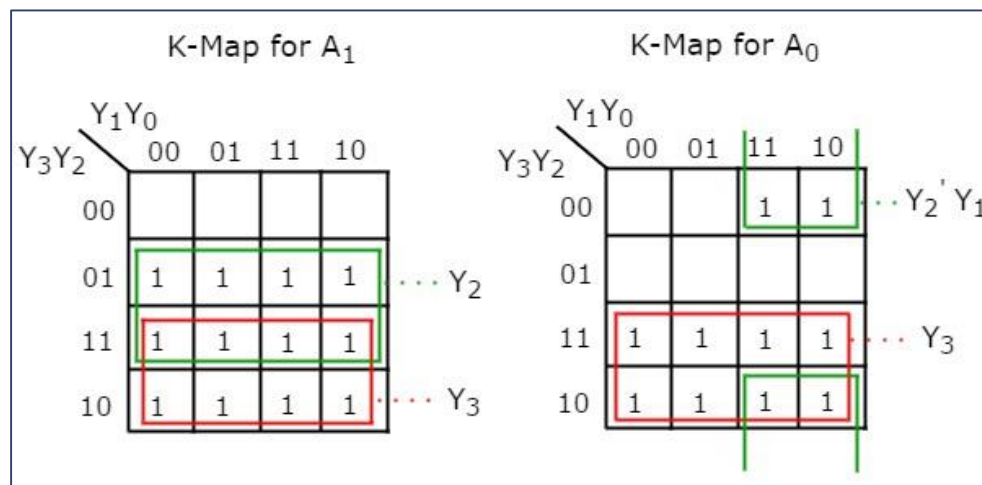

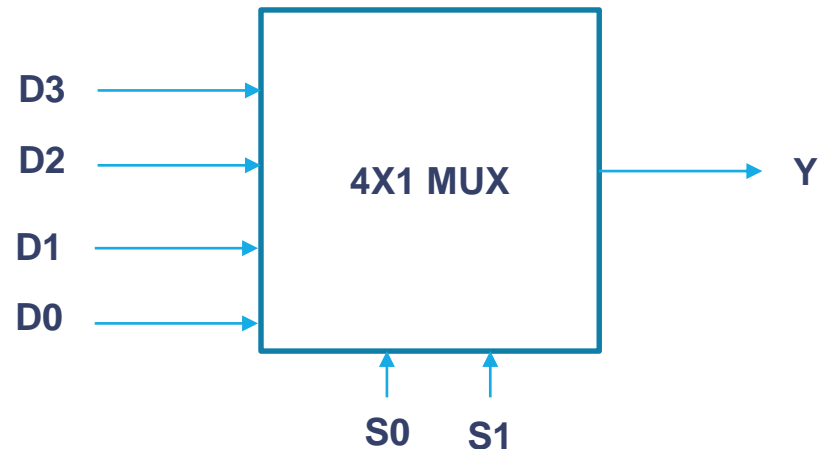
# Multiplexer

- Multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to o/p line. It's also called MUX.
- It is simply a Data Selector.
- How the data is selected?
- There are two selector variables, let  $S_0$  and  $S_1$ .
- MUX will always have 1 output line  $Y$ .
- This is a 4x1 MUX.
- It can also be called as 4:1 MUX.
- So, if no of inputs,  $n=2^m$
- Then,  $m$ =no of selector variables.
- Here,  $n=4$ , so  $m=2$
- Types: 2:1 MUX, 4:1 MUX,
- 8:1 MUX, 16:1 MUX, 32:1 MUX




# Multiplexer

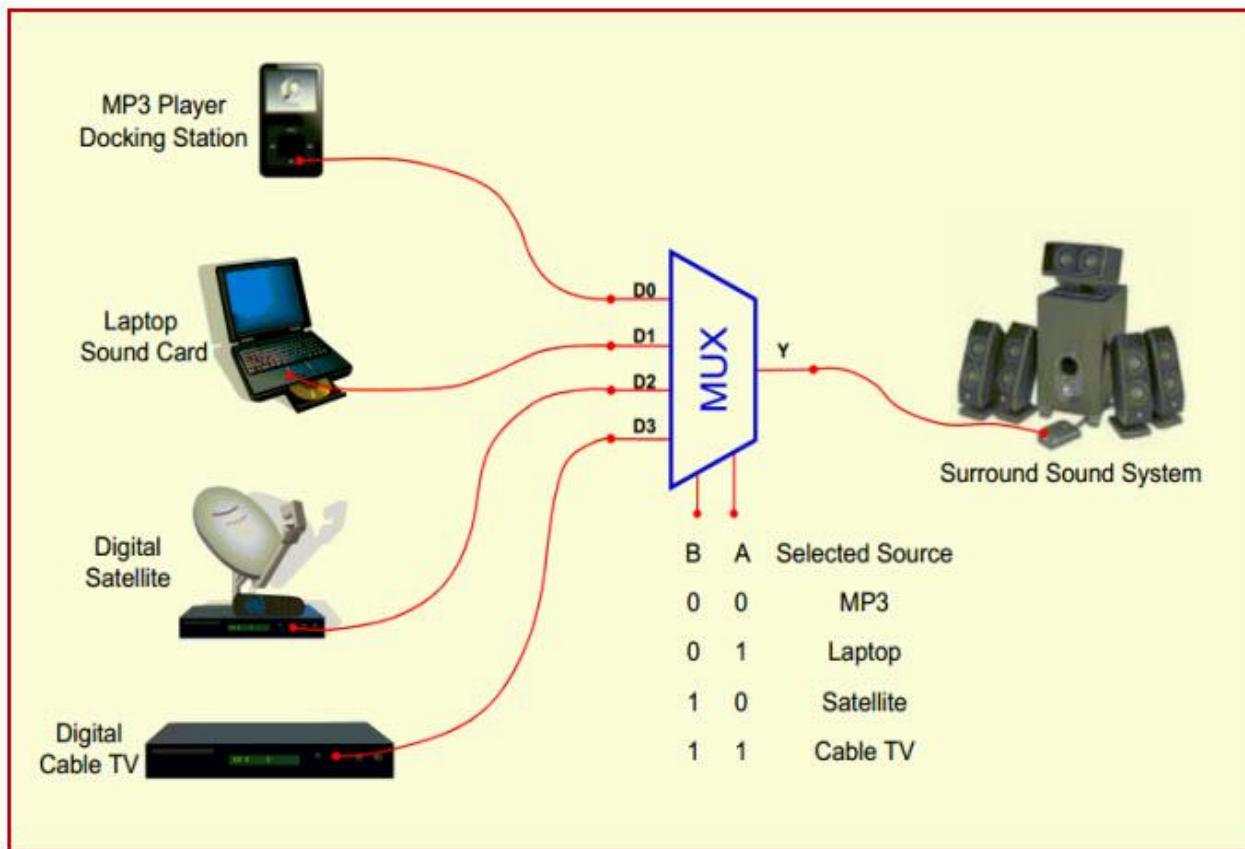
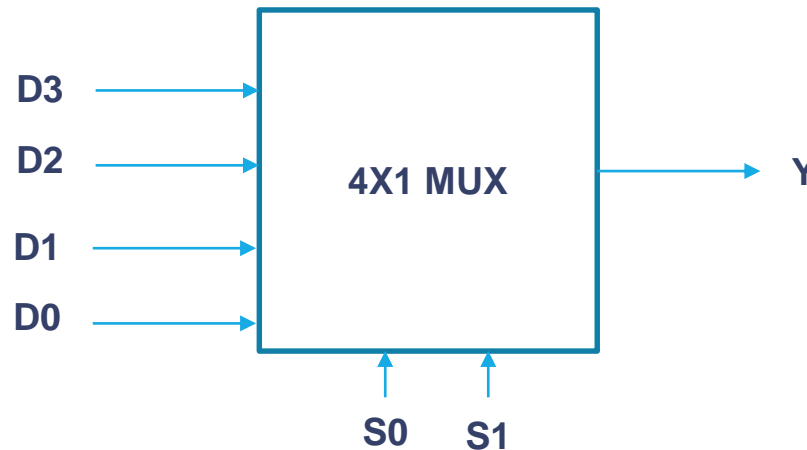
# Advantages of Multiplexer

- Multiplexer is a MSI circuit.
- No of wires are reduced as no of gates are reduced. You can simply connect a no of gates by using a single MUX.
- Reduces circuit complexity and cost as no of gates and wires are reduced.
- Implementation of various circuits using MUX.






# 2x1 Multiplexer


- E is the enable pin. If  $E = 0$ , then whatever the selection pin is, the output  $Y = 0$ . That's why  $S_0 = \text{don't care}$ .
- If  $E = 1$ , then  $Y = \text{input}$ , on the basis of selection pin  $S_0$ .

E	S <sub>0</sub>	Y
0	X	0
1	0	D <sub>0</sub>
1	1	D <sub>1</sub>

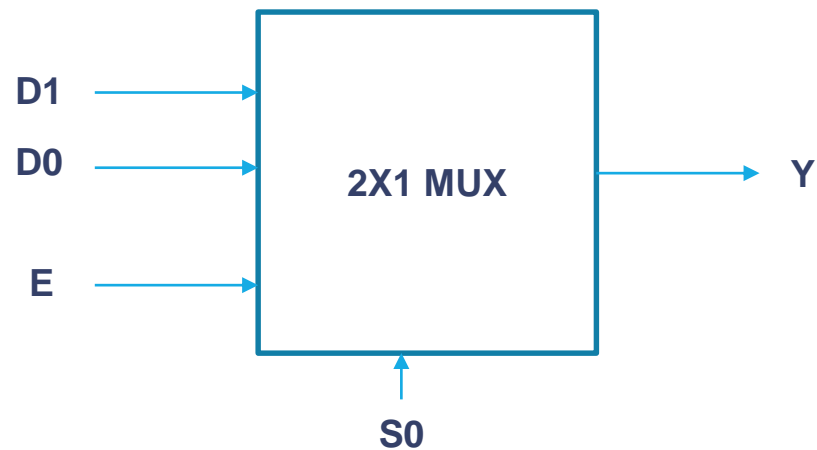

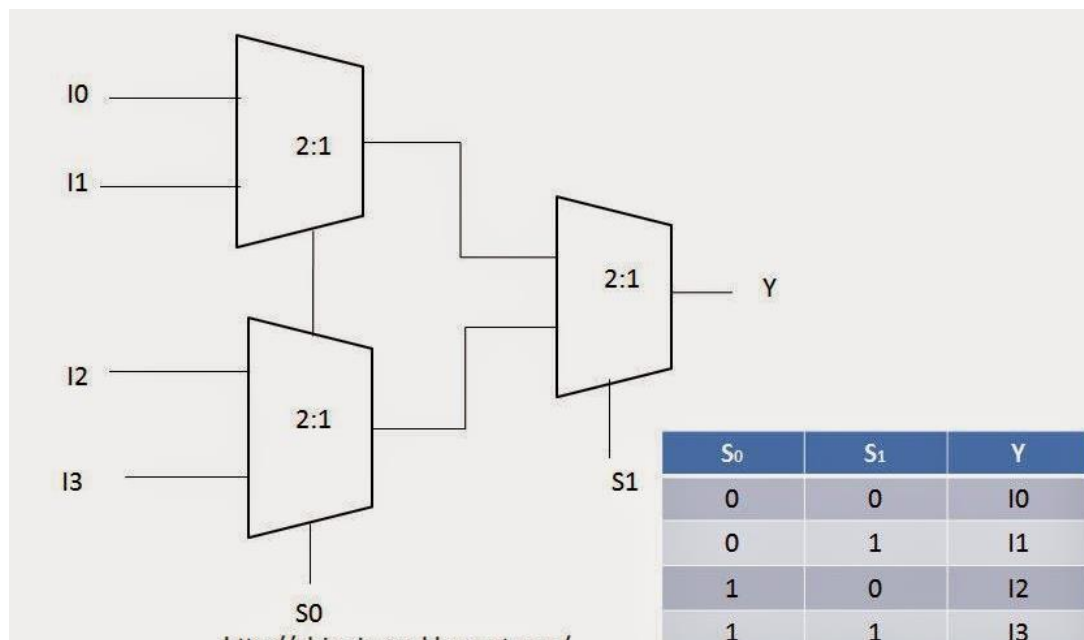
# 4x1 Mux using 2x1 Mux

- $4/2 = 2$
- $2/2 = 1$
- We need total 3 (2x1) MUX



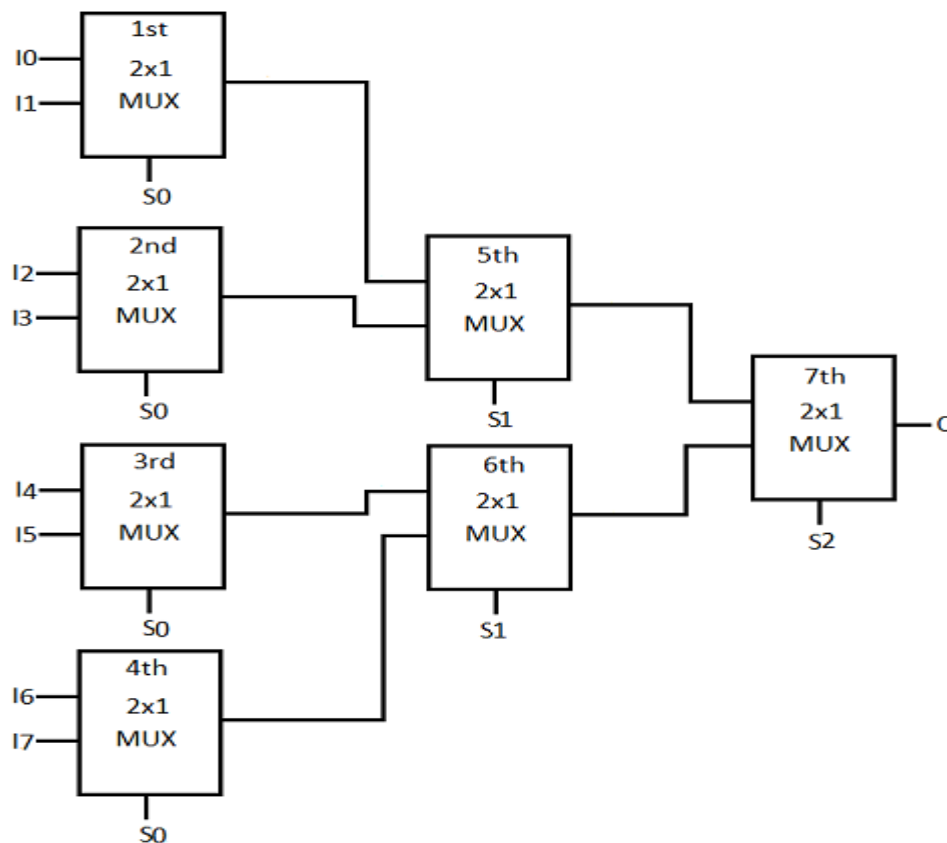
# 8x1 Mux using 2x1 Mux

- $8/2 = 4$
- $4/2 = 2$
- $2/2 = 1$
- We need total 7 (2x1) MUX



# Boolean Function Implementation using MUX

$$F(A, B, C) = \Sigma(1, 3, 5, 6)$$

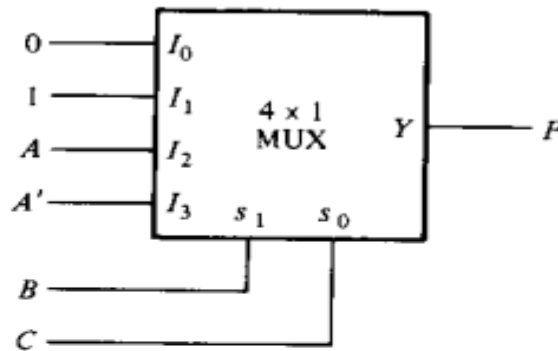

(a) Multiplexer implementation

Minterm	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

(b) Truth table

	$I_0$	$I_1$	$I_2$	$I_3$
$A'$	0	①	2	③
A	4	⑤	⑥	7
	0	1	A	$A'$

(c) Implementation table


**FIGURE 5-18**

# Boolean Function Implementation using MUX

- $F(A,B,C) = \Sigma(1,2,4,5)$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

(a) Truth table

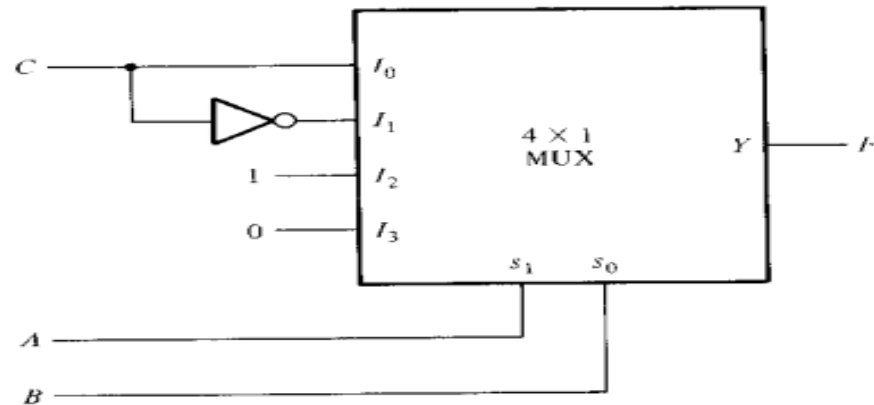

(b) Multiplexer implementation


	$I_0$	$I_1$	$I_2$	$I_3$
$C'$	0	2	4	6
$C$	1	3	5	7
	$C$	$C'$	1	0


(c) Implementation table

# Boolean Function Implementation using MUX

- $F(A,B,C,D) = \Sigma(0,1,3,4,8,9,15)$

	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$A'$	①	①	2	③	④	5	6	7
$A$	⑧	⑨	10	11	12	13	14	⑮
	1	1	0	$A'$	$A'$	0	0	$A$

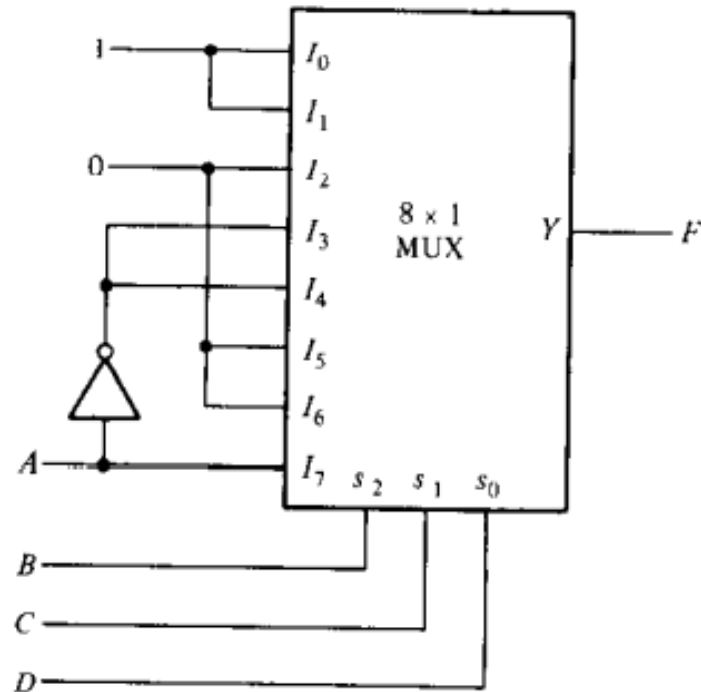



GOOD NEWS!  
THE CLASS IS  
OVER...  
THANK YOU!